

Table of Contents

Introduction	1
About This Book	2
Foolish Assumptions	4
Icons Used in This Book	5
Beyond the Book	5
Where to Go from Here	5
BOOK 1: GETTING STARTED WITH ELECTRONICS	7
CHAPTER 1: Welcome to Electronics	9
What Is Electricity?	10
But Really, What Is Electricity?	12
What Is Electronics?	14
What Can You Do with Electronics?	16
Making noise	16
Making light	17
Transmitting to the world	17
Computing	18
Looking inside Electronic Devices	18
CHAPTER 2: Understanding Electricity	21
Pondering the Wonder of Electricity	22
Looking for Electricity	23
Peering Inside Atoms	24
Examining the Elements	25
Minding Your Charges	26
Conductors and Insulators	27
Understanding Current	28
Understanding Voltage	30
Comparing Direct and Alternating Current	32
Understanding Power	35
CHAPTER 3: Creating Your Mad-Scientist Lab	37
Setting Up Your Mad-Scientist Lab	38
Equipping Your Mad-Scientist Lab	41
Basic hand tools	41
Magnifying glasses	43
Third hands and hobby vises	44
Soldering iron	46
Multimeter	47
Solderless breadboard	49

	Wire	50
	Batteries	51
	Other things to stock up on	53
	Stocking up on Basic Electronic Components	54
	Resistors	54
	Capacitors	55
	Diodes	56
	Light-emitting diodes	57
	Transistors	58
	Integrated circuits	59
	One Last Thing	59
CHAPTER 4:	Staying Safe	61
	Facing the Realities of Electrical Dangers	62
	Household electrical current can kill you!	62
	Even relatively small voltages can hurt you	64
	Sometimes voltage hides in unexpected places	65
	Other Ways to Stay Safe	66
	Keeping Safety Equipment on Hand	69
	Protecting Your Stuff from Static Discharges	69
CHAPTER 5:	Reading Schematic Diagrams	71
	Introducing a Simple Schematic Diagram	72
	Laying Out a Circuit	73
	To Connect or Not to Connect	74
	Looking at Commonly Used Symbols	75
	Simplifying Ground and Power Connections	78
	Labeling Components in a Schematic Diagram	80
	Representing Integrated Circuits in a Schematic Diagram	82
CHAPTER 6:	Building Projects	85
	Looking at the Process of Building an Electronic Project	86
	Envisioning Your Project	87
	Designing Your Circuit	89
	Prototyping Your Circuit on a Solderless Breadboard	94
	Understanding how solderless breadboards work	94
	Laying out your circuit	96
	Assembling the coin-toss circuit on a solderless breadboard	98
	What if it doesn't work?	104
	Constructing Your Circuit on a Printed Circuit Board (PCB)	104
	Understanding how printed circuit boards work	105
	Using a preprinted PCB	106
	Building the coin-toss circuit on a PCB	108

	Finding an Enclosure for Your Circuit	113
	Working with a project box	114
	Mounting the coin-toss circuit in a box	115
CHAPTER 7:	The Secrets of Successful Soldering	121
	Understanding How Solder Works	122
	Procuring What You Need to Solder	123
	Buying a soldering iron	123
	Stocking up on solder	124
	Other goodies you need	125
	Preparing to Solder	126
	Soldering a Solid Solder Joint	127
	Checking Your Work	130
	Desoldering	131
CHAPTER 8:	Measuring Circuits with a Multimeter	133
	Looking at Multimeters	133
	What a Multimeter Measures	137
	Ammeter	137
	Voltmeter	138
	Ohmmeter	138
	Other measurements	139
	Schematic symbols for meter functions	139
	Using Your Multimeter	141
	Measuring current	143
	Measuring voltage	145
	Measuring resistance	146
CHAPTER 9:	Catching Waves with an Oscilloscope	149
	Understanding Oscilloscopes	150
	Examining Waveforms	152
	Calibrating an Oscilloscope	155
	Displaying Signals	157
BOOK 2: WORKING WITH BASIC ELECTRONIC COMPONENTS		161
CHAPTER 1:	Working with Basic Circuits	163
	What Is a Circuit?	164
	Using Batteries	166
	Building a Lamp Circuit	169
	Project 1: A Simple Lamp Circuit	170
	Parts	170
	Steps	170

Working with Switches	171
The many ways to throw the switch	172
Making connections with poles and throws	173
Building a Switched Lamp Circuit	175
Project 2: A Lamp Controlled by a Switch	177
Parts	178
Steps	178
Understand Series and Parallel Circuits	179
Building a Series Lamp Circuit	181
Project 3: A Series Lamp Circuit	181
Parts	182
Steps	183
Building a Parallel Lamp Circuit	183
Project 4: A Parallel Lamp Circuit	184
Parts	185
Steps	185
Using Switches in Series and Parallel	186
Building a Series Switch Circuit	187
Project 5: A Series Switch Circuit	188
Parts	189
Steps	189
Building a Parallel Switch Circuit	190
Project 6: A Parallel Switch Circuit	190
Parts	191
Steps	192
Switching between Two Lamps	193
Project 7: Controlling Two Lamps with One Switch	193
Parts	194
Steps	195
Building a Three-Way Lamp Switch	196
Project 8: A Three-Way Light Switch	198
Parts	198
Steps	199
Reversing Polarity	199
Project 9: A Polarity-Reversing Circuit	200
Parts	201
Steps	201
CHAPTER 2: Working with Resistors	203
What Is Resistance?	204
Measuring Resistance	204
Looking at Ohm's Law	206
Introducing Resistors	208
Reading Resistor Color Codes	209
Reading a resistor's value	210
Understanding resistor tolerance	211

Understanding Resistor Power Ratings	213
Limiting Current with a Resistor	214
Project 10: Using a Current-Limiting Resistor	216
Parts	217
Steps	217
Combining Resistors	218
Combining resistors in series	219
Combining resistors in parallel	220
Mixing series and parallel resistors	221
Combining resistors in series and parallel	223
Project 11: Resistors in Series and Parallel	223
Parts	223
Steps	225
Dividing Voltage	228
Dividing Voltage with Resistors	229
Project 12: A Voltage Divider Circuit	229
Parts	230
Steps	231
Varying Resistance with a Potentiometer	232
CHAPTER 3: Working with Capacitors	235
What Is a Capacitor?	236
Counting Capacitance	239
Reading Capacitor Values	240
The Many Sizes and Shapes of Capacitors	242
Calculating Time Constants for Resistor/Capacitor Networks	245
Combining Capacitors	247
Combining capacitors in parallel	248
Connecting capacitors in series	248
Putting Capacitors to Work	250
Charging and Discharging a Capacitor	250
Project 13: Charging and Discharging a Capacitor	251
Parts	252
Steps	253
Blocking DC while Passing AC	254
Project 14: Blocking Direct Current	256
Parts	257
Steps	258
CHAPTER 4: Working with Inductors	261
What Is Magnetism?	262
The north and south of magnetism	263
Pondering permanent magnets	264
Examining Electromagnets	264

	Inducing Current	265
	Inductance and the art of resisting change	266
	Regarding henry	268
	Calculating RL Time Constants	269
	Calculating Inductive Reactance	271
	Combining Inductors	271
	Putting Inductors to Work	272
CHAPTER 5:	Working with Diodes and LEDs	275
	What Is a Semiconductor?	276
	Doping: It's not just for athletes	278
	Understanding p-n junctions	279
	Introducing Diodes	281
	The Many Types of Diodes	283
	Rectifier diodes	283
	Signal diodes	284
	Zener diodes	284
	Using a Diode to Block Reverse Polarity	286
	Project 15: Blocking Reverse Polarity	286
	Parts	287
	Steps	287
	Putting Rectifiers to Work	289
	Building Rectifier Circuits	291
	Project 16: Rectifier Circuits	292
	Parts	293
	Steps	293
	Introducing Light Emitting Diodes	294
	Using LEDs to Detect Polarity	297
	Project 17: An LED Polarity Detector	298
	Parts	298
	Steps	299
CHAPTER 6:	Working with Transistors	301
	What's the Big Deal about Transistors?	302
	Why were transistors invented?	303
	Looking inside a transistor	304
	Examining transistor specifications	307
	Amplifying with a Transistor	308
	Using a Transistor as a Switch	312
	An LED Driver Circuit	314
	Project 18: A Transistor LED Driver	315
	Parts	316
	Steps	317
	Looking at a Simple NOT Gate Circuit	318
	Building a NOT Gate	319

Project 19: A NOT Gate	319
Parts	321
Steps	321
Oscillating with a Transistor	323
Building an LED Flasher	325
Project 20: An LED Flasher	327
Parts	328
Steps	328
Wrapping Up Our Exploration of Discrete Components	330
BOOK 3: WORKING WITH INTEGRATED CIRCUITS	331
CHAPTER 1: Introducing Integrated Circuits	333
What Exactly Is an Integrated Circuit?	334
Looking at How Integrated Circuits Are Made	335
Integrated Circuit Packages	336
Using ICs in Schematic Diagrams	339
Powering ICs.	340
Avoiding Static and Heat Damage.	341
Reading IC Data Sheets.	342
Popular Integrated Circuits	343
555 Timer	343
741 and LM324 Op-Amp.	344
78xx Voltage Regulator.	344
74xx Logic Family.	344
CHAPTER 2: The Fabulous 555 Timer Chip	345
Looking at How the 555 Works	346
Understanding 555 Modes.	348
Using the 555 in Monostable (One-Shot) Mode	349
Looking at a typical 555 monostable circuit	349
Looking at the resistor-capacitor circuit in a monostable timer	350
Calculating the time interval for a monostable circuit.	351
Using the 555 in Astable (Oscillator) Mode	352
Looking at a typical astable circuit	353
Controlling the time intervals in an astable 555 circuit	354
Calculating the duty cycle.	356
Using the 555 in Bistable (Flip-Flop) Mode	357
Using the 555 Timer Output	359
Doubling Up with the 556 Dual Timer	361
Making a One-Shot Timer.	364
Project 21: A One-Shot 555 Timer Circuit.	366
Parts	366
Steps	367

Making an LED Flasher	369
Project 22: An LED Flasher	370
Parts	371
Steps	372
Using a Set/Reset Switch	373
Project 23: An LED Flasher with a Set/Reset Switch	374
Parts	375
Steps	376
Making a Beeper	377
Project 24: An Audible Beeper	379
Parts	379
Steps	380
CHAPTER 3: Working with Op-Amps	383
Looking at Operational Amplifiers	384
Understanding Open Loop-Amplifiers	388
Looking at Closed Loop-Amplifiers	391
Using an Op-Amp as a Unity Gain Amplifier	393
Configuring a unity follower	394
Configuring a unity inverter	394
Using an Op-Amp as a Voltage Comparator	395
Adding Voltages	398
Working with Op-Amp ICs	401
BOOK 4: BEYOND DIRECT CURRENT	403
CHAPTER 1: Getting into Alternating Current	405
What Is Alternating Current?	406
Measuring Alternating Current	408
Understanding Alternators	411
Understanding Motors	413
Understanding Transformers	413
Working with Line Voltage	416
Using Line Voltage in Your Projects	417
Being safe with line voltage	418
Understanding hot, neutral, and ground	419
Wires and Connectors for Working with Line Voltage	421
Using Fuses to Protect Line-Voltage Circuits	423
Using Relays to Control Line-Voltage Circuits	425
CHAPTER 2: Building Power Supplies	429
Using a Power Adapter	430
Understanding What a Power Supply Does	431
Transforming Voltage	432
Turning AC into DC	433

	Half-wave rectifier	434
	Full-wave rectifier	435
	Bridge rectifier	435
	Filtering Rectified Current	436
	Regulating Voltage	438
CHAPTER 3:	Understanding Radio	441
	Understanding Radio Waves	442
	Transmitting and Receiving Radio	445
	Understanding radio transmitters	445
	Understanding radio receivers	446
	Understanding AM Radio	449
	Understanding FM Radio	451
	Building a Crystal Radio	454
	Looking at a simple crystal radio circuit	455
	Gathering your parts	456
	Building the coil	457
	Assembling the circuit	460
	Stringing up an antenna	462
	Connecting to ground	464
	Using the crystal radio	465
CHAPTER 4:	Working with Infrared	467
	Introducing Infrared Light	467
	Detecting Infrared Light	469
	Project 25: A Simple IR Detector	471
	Parts	472
	Steps	472
	Creating Infrared Light	473
	Building a Proximity Detector	475
	Building a Common-Emitter Proximity Detector	476
	Project 26: A Common-Emitter Proximity Detector	477
	Parts	479
	Steps	479
	Building a Common-Collector Proximity Detector	480
	Project 27: A Common-Collector Proximity Detector	482
	Parts	483
	Steps	483
	BOOK 5: DOING DIGITAL ELECTRONICS	485
CHAPTER 1:	Understanding Digital Electronics	487
	Distinguishing Analog and Digital Electronics	487
	Understanding Binary	490
	Knowing your number systems	490

Counting by ones.	490
Doing the logic thing.	493
Using Switches to Build Gates.	495
Project 28: A Simple AND Circuit.	497
Parts	497
Steps	498
Project 29: A Simple OR Circuit	499
Parts	499
Steps	500
Project 30: A Simple XOR Circuit	501
Parts	502
Steps	502
CHAPTER 2: Getting Logical	503
Introducing Boolean Logic and Logic Gates	504
Looking at NOT Gates.	505
Looking at AND Gates.	506
Looking at OR Gates	509
Looking at NAND Gates	511
Looking at NOR Gates.	513
Looking at XOR and XNOR Gates	514
De Marvelous De Morgan's Theorem.	516
All You Need Is NAND (Or NOR)	519
Universal NAND gates.	519
Universal NOR gates	520
Using Software to Practice with Gates	521
CHAPTER 3: Working with Logic Circuits.	523
Creating Logic Gates with Transistors	523
A transistor NOT gate circuit	524
Project 31: A Transistor NOT Gate	525
Parts	527
Steps	527
A transistor AND gate circuit	528
A transistor NAND gate circuit.	529
Project 32: A Transistor NAND Gate	530
Parts	532
Steps	532
A transistor OR gate circuit	534
A transistor NOR gate circuit	534
Project 33: A Transistor NOR Gate	536
Parts	537
Steps	538
Introducing Integrated Circuit Logic Gates	539
Introducing the Versatile 4000-Series Logic Gates	542

Building Projects with the 4011 Quad Two-Input NAND Gate	544
Project 34: A CMOS NAND Gate	546
Parts	547
Steps	547
Project 35: A CMOS AND Gate	549
Parts	550
Steps	551
Project 36: A CMOS OR Gate	552
Parts	554
Steps	554
Project 37: A CMOS NOR Gate	556
Parts	557
Steps	557
CHAPTER 4: Working with Flip-Flops	561
Looking at Latches	562
Project 38: An Active-High Latch	566
Parts	567
Steps	567
Project 39: An Active-Low Latch	569
Parts	570
Steps	570
Looking at Gated Latches	572
Project 40: A Gated D Latch	575
Parts	576
Steps	576
Introducing Flip-Flops	579
Project 41: A D Flip-Flop	582
Parts	584
Steps	584
Project 42: A Toggle Flip-Flop	586
Parts	588
Steps	588
Debouncing a Clock Input	589
CHAPTER 5: Introducing Microcontrollers	591
Introducing Microcontrollers	592
Programming a Microcontroller	593
Working with I/O Pins	594
BOOK 6: WORKING WITH ARDUINO	
MICROPROCESSORS	597
CHAPTER 1: Introducing Arduino	599
Introducing the Arduino UNO	599
Buying an UNO Starter Kit	603

	Installing the Arduino IDE	603
	Connecting to an UNO	604
	Looking at a Simple Arduino Sketch	605
	Running the Blink Program	607
	Using a Digital I/O Pin to Control an LED	608
	Project 43: Blinking an LED with an Arduino UNO	612
	Parts	613
	Steps	613
CHAPTER 2:	Creating Arduino Sketches	615
	Introducing C	616
	Working with a Prototyping Shield	619
	Building a Test Circuit	621
	Project 44: An Arduino LED Test Circuit	622
	Parts	623
	Steps	623
	Flashing the LEDs	625
	Using Comments	627
	Creating Identifiers	629
	Using Variables	629
	Doing Math	631
	A Program That Uses Variables and Math	632
	Using If Statements	634
	Using While Loops	638
	Using For Loops	641
	Crafting Your Own Functions	644
CHAPTER 3:	More Arduino Programming Tricks	647
	Using a Push Button with an Arduino	647
	Checking the Status of a Switch in Arduino	649
	Project 45: A Push-Button Controlled Arduino LED Flasher	652
	Parts	653
	Steps	654
	Randomizing Your Programs	655
	Reading a Value from a Potentiometer	658
	Project 46: A Variable-Rate LED Flasher	660
	Parts	662
	Steps	662
CHAPTER 4:	An Arduino Proximity Sensor	665
	Using an Ultrasonic Range Finder	665
	Looking at the HC-SR04 Range Finder	666
	Generating a trigger pulse	667
	Reading pulse input	668

Doing the math	668
Using an LCD	669
Connecting an LCD to Arduino	670
Programming the LCD	671
Building a Proximity Sensor	673
Project 47: An Arduino Proximity Sensor	674
Parts	675
Steps	676
CHAPTER 5: Adding Sound and Motion to Your Arduino Projects	681
Using a Speaker with an Arduino	681
Using the tone function	683
Connecting a speaker to an Arduino	684
Project 48: Creating Sound with a Speaker	686
Parts	687
Steps	687
Sounding the alarm with Morse code	688
Playing a siren	690
Playing a song	692
Using an MP3 Shield	694
Assembling the Music Maker shield	695
Preparing the micro-SD card	695
Programming the Music Maker shield	696
Building an Arduino Music Player	699
Project 49: Using a Music Maker Shield to Play Sounds	699
Parts	700
Steps	700
Using a Servo with an Arduino	702
Connecting a servo to an Arduino	702
Programming a servo	704
Building a servo project	707
Project 50: Using a Servo with an Arduino	707
Parts	709
Steps	709
CHAPTER 6: Keypads and Keyboards	711
Using a Keypad	711
How a keypad works	712
Connecting a keypad to an Arduino	713
Programming a keypad	714
Setting Up a Keypad	716

Defining the number of rows and columns.....	717
Defining the row and column pins.....	717
Defining the keymap.....	718
Using a Keypad variable.....	718
Detecting when a key has been pressed.....	719
Building a Keypad Circuit.....	720
Project 51: Using a Keypad.....	720
Parts.....	721
Steps.....	722
Using an Arduino for Computer Keyboard Input.....	724
Using the Keyboard library.....	725
Sending a line via the keyboard.....	726
Using the switch statement to simplify choices.....	727
Pressing and holding keys.....	728
Building a Windows Keypad Gadget.....	730
Project 52: A Windows Keypad Gadget.....	730
Parts.....	731
Steps.....	731

BOOK 7: WORKING WITH RASPBERRY PI..... 735

CHAPTER 1: Introducing Raspberry Pi..... 737

Introducing the Raspberry Pi.....	738
Considering Raspberry Pi Versions.....	740
Setting Up a Raspberry Pi.....	741
Installing the Raspberry Pi Operating System.....	742
Starting Up Your Raspberry Pi.....	744
Understanding the File System.....	746
Writing Your First Raspberry Pi Program.....	748
Examining GPIO Ports.....	751
Connecting an LED to a GPIO Port.....	753
Flashing an LED in Python.....	754
Building a Raspberry Pi LED Flasher.....	755
Project 51: Blinking an LED with a Raspberry Pi.....	756
Parts.....	757
Steps.....	758

CHAPTER 2: Programming in Python..... 759

Looking Closer at Python.....	760
Building a Test Circuit.....	761
Project 52: A Raspberry Pi LED Test Board.....	762
Parts.....	763
Steps.....	764
Flashing the LEDs.....	765
Using Comments.....	768
Creating Identifiers.....	770

	Using Constants	770
	Using Variables	772
	Creating Your Own Functions	775
	Using If Statements	778
	Using While Loops	781
	Using For Loops	784
	Looking at Python Lists	787
CHAPTER 3:	Reading Digital and Analog Input	791
	Using a GPIO Port for Digital Input	791
	Checking the Status of a Switch in Python	794
	Project 53: A Push-Button-Controlled Raspberry Pi LED Flasher	796
	Parts	798
	Steps	798
	Reading Analog Input	799
	Enabling SPI on Your Raspberry Pi	803
	Using the MCP3008 in Python	804
	Using the mcp3008 Package	805
	Project 54: A Variable-Rate LED Flasher	808
	Parts	809
	Steps	810
	BOOK 8: SPECIAL EFFECTS	813
CHAPTER 1:	Building a Color Organ	815
	Examining the Color Organ Project	816
	Understanding How the Color Organ Works	818
	Getting What You Need to Build the Color Organ	819
	Assembling the Color Organ	819
	Using the Color Organ	825
CHAPTER 2:	Animating Holiday Lights	827
	Introducing the ShowTime PC Controller	828
	Looking at a Basic Light-O-Rama Setup	830
	Understanding Channels and Sequences	832
	Choosing Lights for Your Display	833
	Designing Your Layout	835
	Assembling the ShowTime PC Controller	835
	Connecting the Controller to a Computer	837
	Testing the ShowTime PC Controller	838
	Using the Light-O-Rama Sequence Editor	840
	Understanding Sequences	841
	Creating a Musical Sequence	842
	Visualizing Your Show	847

CHAPTER 3: Building an Animatronic Prop Controller	851
Looking at the Requirements of Animatronic Prop Control	852
Examining a Typical Animatronic Prop	854
Building the Prop Controller	858
Programming the Prop-1 Controller	863
Sending Commands to the RC-4 or AP-16+ Modules	864
Programming the RC-4 Relay Control Module	866
Turning all relays off	867
Turning an individual relay on or off	867
Setting all four relays at once	868
Using symbols to make RC-4 commands more readable	869
A sample program for controlling all four RC-4 relays	869
Programming the AP-16+ Audio Player Module	871
Resetting the AP-16+	873
Changing the volume	874
Playing a specific file	874
Waiting for a file to finish playing	875
A Sample AP-16+ Program	876
Programming the PIR Motion Detector	877
Looking at Complete Jack-in-the-Box Program	878
CHAPTER 4: Re-Creating a Retro Science-Fiction Robot Head ..	881
Looking to Robby and B-9 For Inspiration	882
Conceiving VIN-e	884
Introducing VIN-e 1.0	885
The dome	885
The base	886
The central pillar	886
The eyes and nose	887
The mouth	888
The "vacuum tubes"	888
The antenna	889
Looking at VIN-e's Electronics	889
A Final Word about Safety	891
INDEX	893