

CONTENTS

Laplace Transform Theory	1
Experiment 1: Transfer Functions	29
Experiment 2: Frequency Response and Bode Plots	39
Experiment 3: Asymptotic Bode Plots; Lead and Lag Networks	47
Experiment 4: Transients in DC Networks	59
Experiment 5: Transients in AC Networks	69
Experiment 6: Initial Conditions	81
Experiment 7: Mesh Analysis	91
Experiment 8: Superposition	103
Experiment 9: The Initial and Final Value Theorems	115
Experiment 10: The Shifting Theorem	125
Appendix	133